


EDGE DETECTOR

Positive edge detector:


Verilog code:

```
module posedge_detector(  
    input wire clk,  
    input wire signal_in,  
    output reg pos_edge_out  
);  
    reg signal_d;  
    always @(posedge clk) begin  
        signal_d <= signal_in;  
        pos_edge_out <= signal_in & ~signal_d;  
    end  
endmodule
```


Waveform:

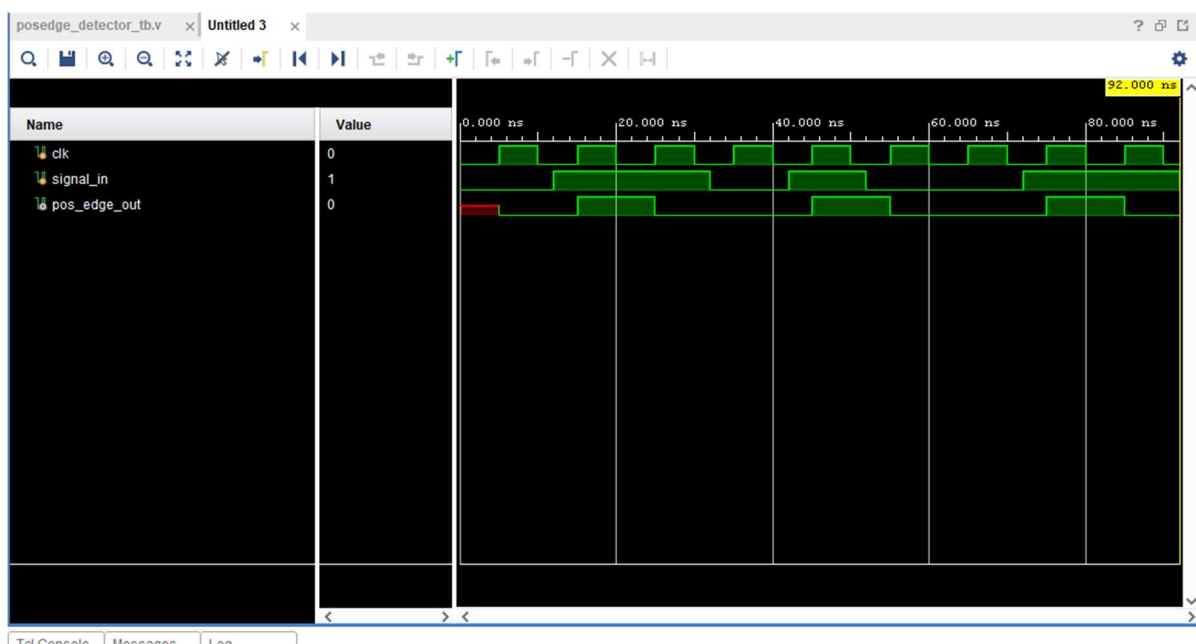

RTL analysis:

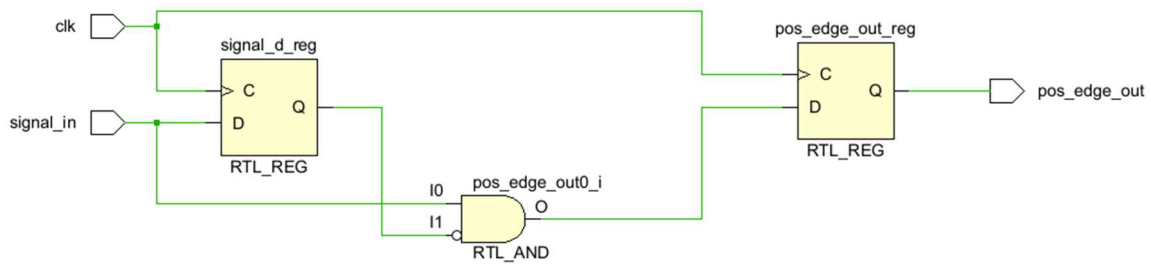

Synthesis schematic:

 

Look Up Table:

Cell Properties

pos_edge_out_i_1


I1	I0	O=I0 & !I1
0	0	0
0	1	1
1	0	0
1	1	0

Both edge detector:


Verilog code:

```
module both_edgedetector (  
    input wire clk,  
    input wire signal_in,  
    output reg pos_edge_out,  
    output reg neg_edge_out  
);  
    reg signal_d;  
    always @(posedge clk) begin  
        signal_d <= signal_in;  
        pos_edge_out <= signal_in & ~signal_d;  
        neg_edge_out <= ~signal_in & signal_d;  
    end  
endmodule
```


Waveform:

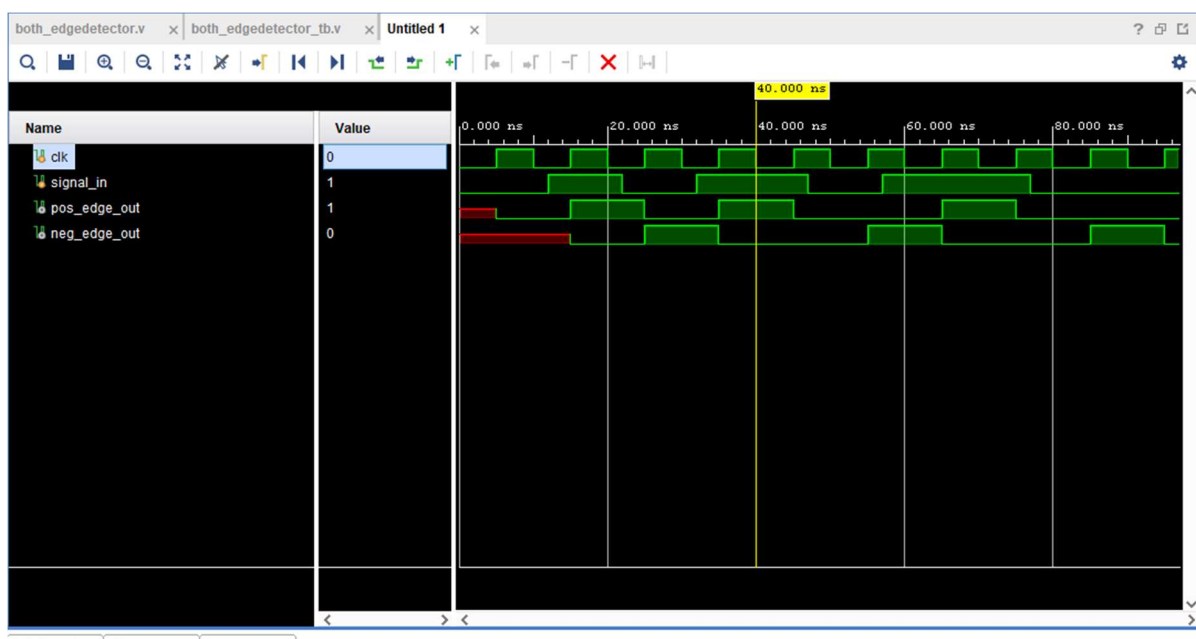

RTL schematic:

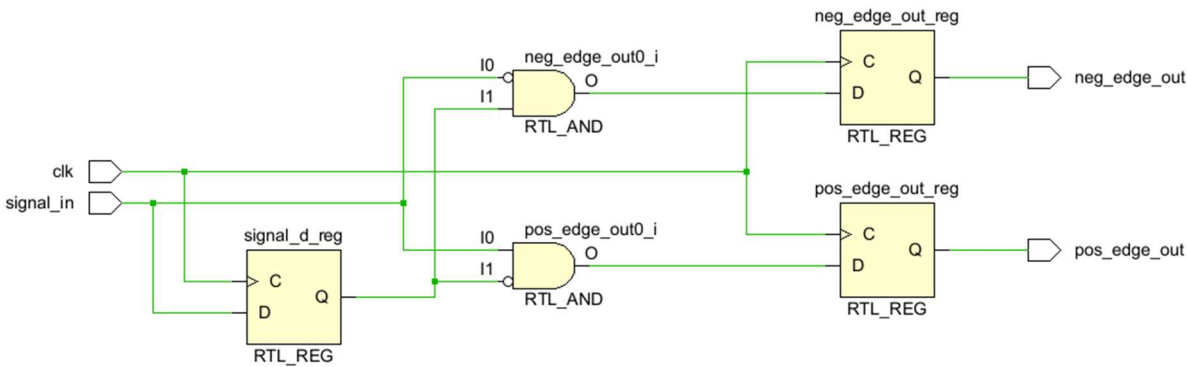

Synthesis schematic:

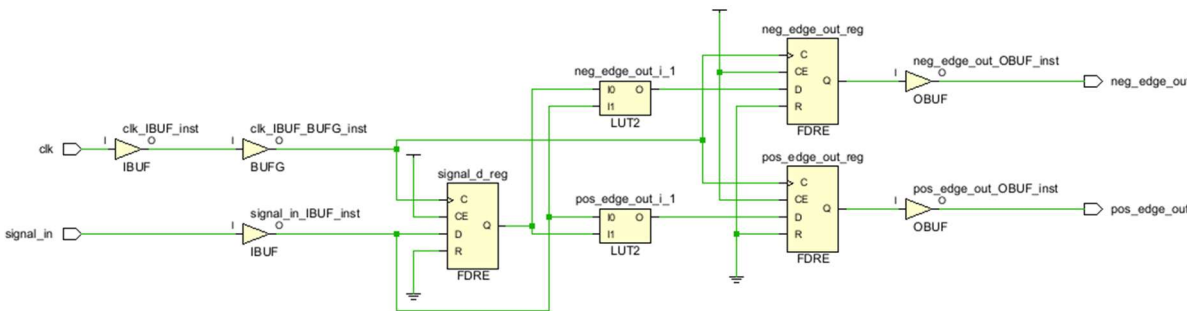

Look Up Table:

Cell Properties

pos_edge_out_i_1

I1	I0	O=I0 & !I1
0	0	0
0	1	1
1	0	0
1	1	0

Cell Properties

neg_edge_out_i_1

I1	I0	O=I0 & !I1
0	0	0
0	1	1
1	0	0
1	1	0

