


MEMORIES

Single port BRAM (16 X 2048)


Verilog code:

```
module singleport_BRAM(  
    input clk,  
    input we,  
    input [10:0] addr,  
    input [15:0] din,  
    output reg [15:0] dout  
);  
(* ram_style = "block" *)  
reg [15:0] mem [0:2047];  
always @(posedge clk) begin  
    if (we) begin  
        mem[addr] <= din;  
    end  
    dout <= mem[addr];  
end  
endmodule
```

RTL schematic:

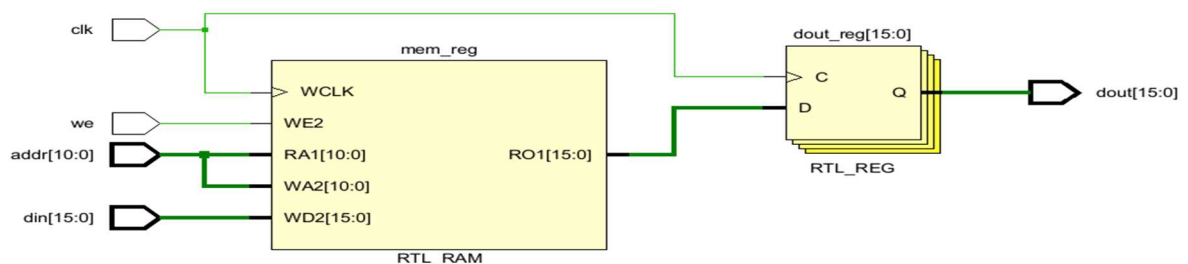

Synthesis schematic:

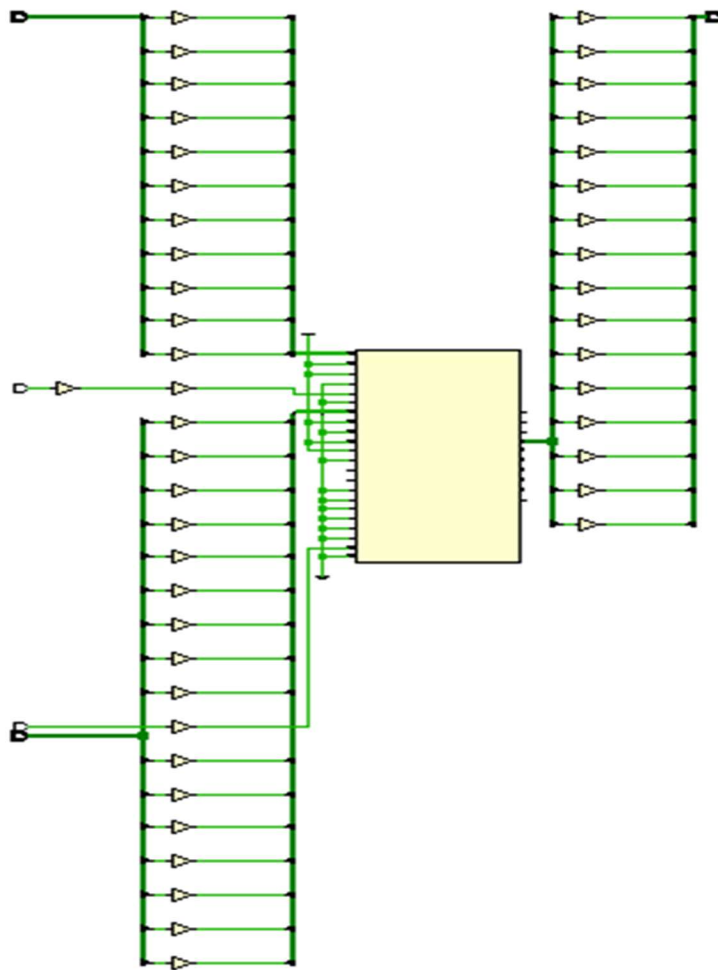

2. Memory

Site Type	Used	Fixed	Prohibited	Available	Util%
Block RAM Tile	1	0	0	140	0.71
RAMB36/FIFO*	1	0	0	140	0.71
RAMB36E1 only	1				
RAMB18	0	0	0	280	0.00

* Note: Each Block RAM Tile only has one FIFO logic available and therefore can accomm


ONE 36K BRAM is needed since $(16 \times 2048 = 32768)$ less than $36K = 36 \times 1024 = 36864$ of
RAMB36E1

True dual port BRAM (32X16K)


Verilog code:

```
module truedualport_BRAM (  
    input clka,  
    input clkb,  
    input wea,  
    input web,  
    input [8:0] addra,  
    input [8:0] addrb,  
    input [31:0] dina,  
    input [31:0] dinb,  
    output reg [31:0] douta,  
    output reg [31:0] doutb  
);  
(* ram_style = "block" *)  
reg [31:0] mem [0:511]; // locations ( 16K = 16384) 16384 /32 = 512 words  
always @(posedge clka) begin  
    if (wea)  
        mem[addra] <= dina;  
    douta <= mem[addra];  
end  
always @(posedge clkb) begin  
    if (web)  
        mem[addrb] <= dinb;  
    doutb <= mem[addrb];  
end  
endmodule
```

RTL schematic:

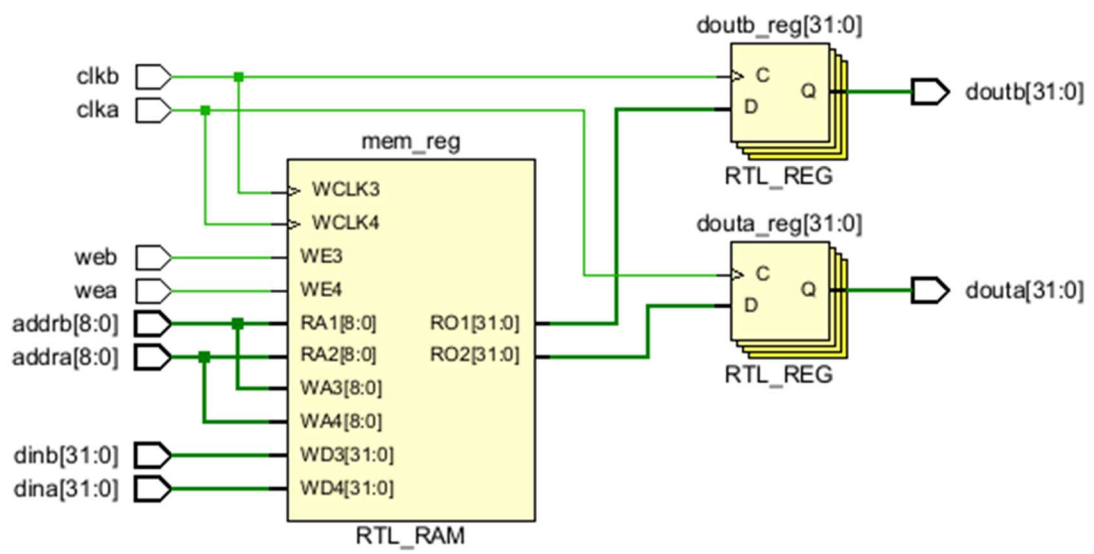

Synthesis schematic:

 


Distributed BRAM (256 X 32)

Verilog code:

```
module distributed_BRAM (  
    input clk,  
    input we,  
    input [7:0] addr,  
    input [31:0] din,  
    output reg [31:0] dout  
);  
  
(* ram_style = "distributed" *)  
reg [31:0] mem [0:255];  
  
always @(posedge clk) begin  
    if (we)  
        mem[addr] <= din;  
    dout <= mem[addr];  
  
end  
endmodule
```

RTL schematic:

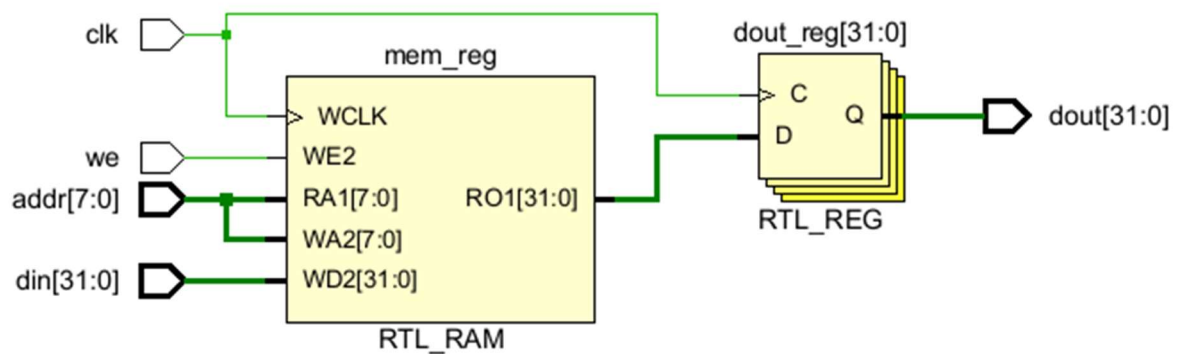

2. Memory

Site Type	Used	Fixed	Prohibited	Available	Util%
Block RAM Tile	0	0	0	140	0.00
RAMB36/FIFO*	0	0	0	140	0.00
RAMB18	0	0	0	280	0.00

1. Slice Logic

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	128	0	0	53200	0.24
LUT as Logic	0	0	0	53200	0.00
LUT as Memory	128	0	0	17400	0.74
LUT as Distributed RAM	128	0			
LUT as Shift Register	0	0			
Slice Registers	32	0	0	106400	0.03
Register as Flip Flop	32	0	0	106400	0.03
Register as Latch	0	0	0	106400	0.00
F7 Muxes	64	0	0	26600	0.24
F8 Muxes	32	0	0	13300	0.24