 


AND GATE WITH D FLIP FLOP


Verilog code:

```
module and_gate_d(input wire clk,  
    input wire a,  
    input wire b,  
    output reg y  
);  
always @(posedge clk) begin  
    y <= a & b;  
end  
endmodule
```

RTL analysis schematic:



Synthesis schematic:

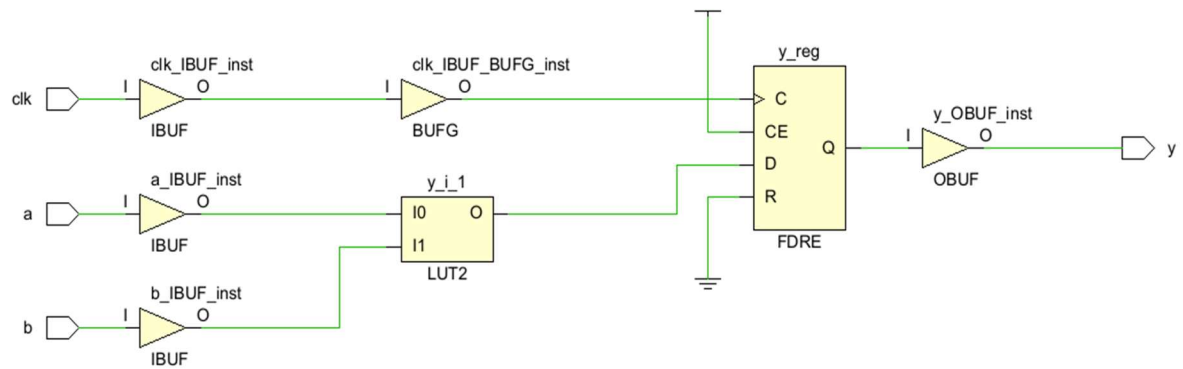

Look Up Table:

Cell Properties

■ `y_i_1`

I1	I0	O=I0 ...
0	0	0
0	1	0
1	0	0
1	1	1