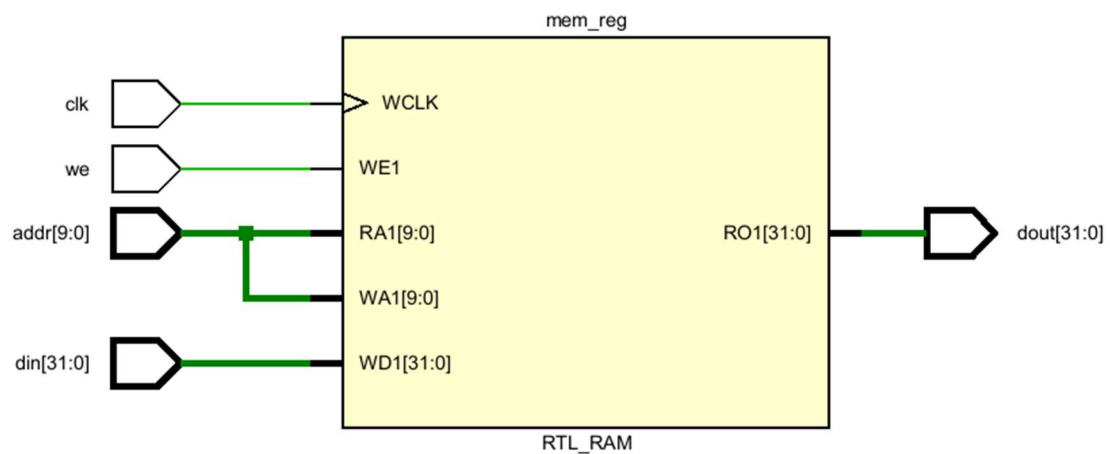


BRAM


Verilog code:

```
module BRAM (  
    input clk,  
    input we,  
    input [9:0] addr,  
    input [31:0] din,  
    output [31:0] dout  
);  
    reg [31:0] mem [0:1023];  
    always @(posedge clk) begin  
        if(we) begin  
            mem[addr]<=din;  
        end  
    end  
    assign dout = mem[addr];  
endmodule
```

RTL schematic:



Synthesis schematic:

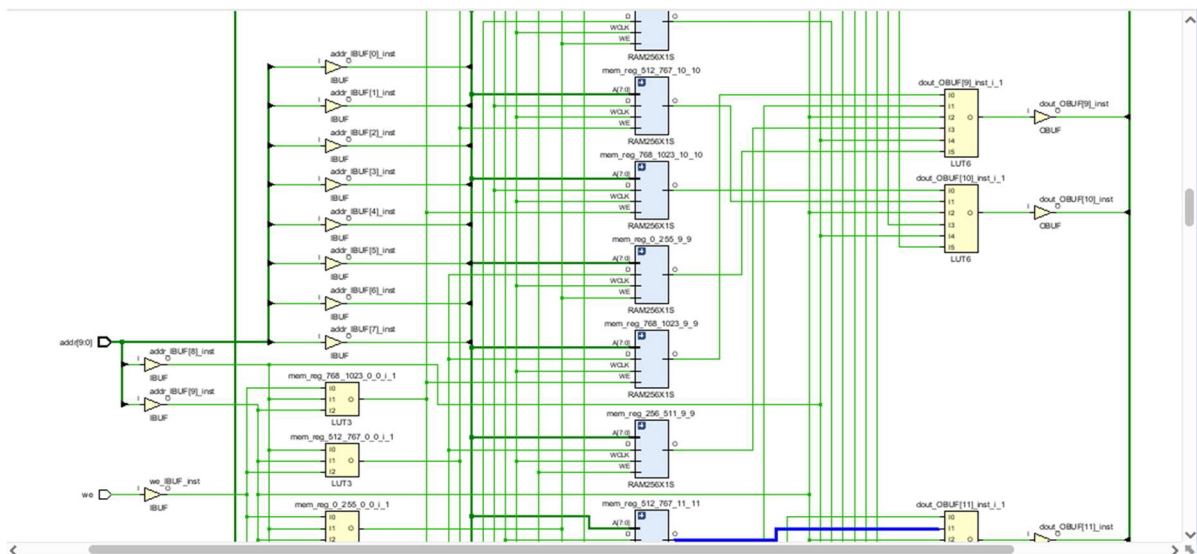

It uses LUT resources (LUT3 AND LUT6)